

Fundamentals of Electronic Circuits and Systems I

Capacitor & Inductor

Milin Zhang

Dept of EE, Tsinghua University




Outlines


- Capacitor
- Inductor
- Magnetically coupled networks

What is a capacitor?

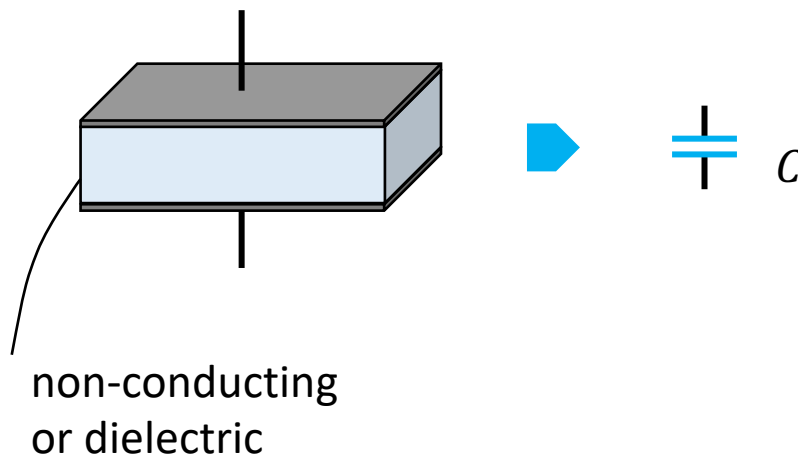A CAPACITOR is a circuit element that consists of two conducting surface separated by a non-conducting, or dielectric, material.



What is a capacitor?

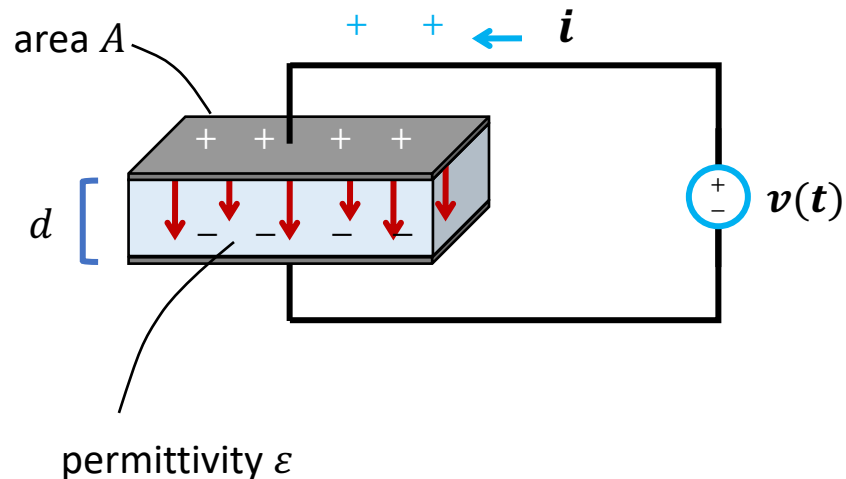


- Step 1: Voltage difference $v(t)$ applied between the two conductors
- Step 2: Charge $q(t)$ is transferred from the source to the capacitor
- Step 3: an electric field across dielectric is created, with a strength of

$$E(t) = \frac{q(t)}{\epsilon A}$$

electric field $E(t)$ is proportional to charges $q(t)$ on conductors

What is a capacitor?

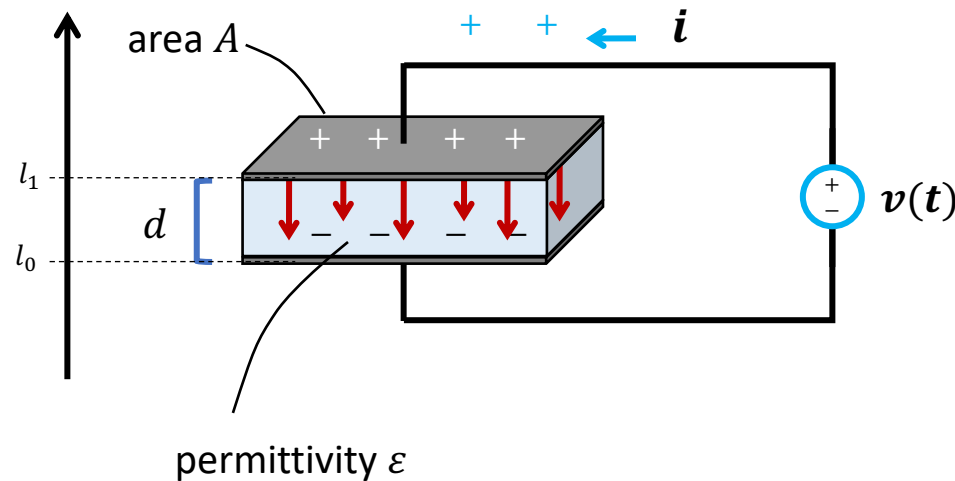

The voltage between two surfaces

$$v(t) = \int_{l_0}^{l_1} E(t) dl = E(t)l(t)$$

The charge on the capacitor


$$q(t) = E(t)\epsilon A = \frac{v(t)}{l(t)}\epsilon A = \boxed{\frac{\epsilon A}{l(t)}} v(t)$$

$C(t)$

Potential difference $v(t)$ between conductors is proportional to charges $q(t)$ on conductors

What is a capacitor?

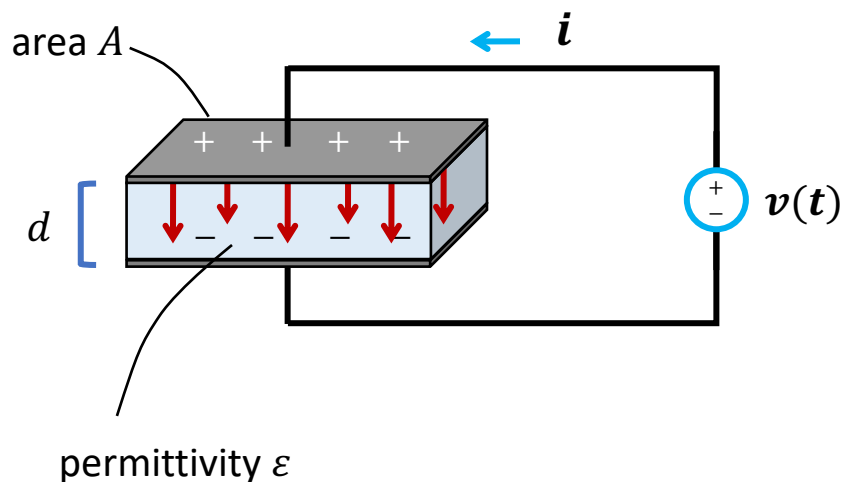
CAPACITANCE of two parallel plates separated by air



$$C = \varepsilon_0 \frac{A}{d}$$

- The unit of capacitance: **farad (F)**
- More frequently used: **μF , pF**
- $\varepsilon_0 = 8.85 \times 10^{-12} F/m$, the permittivity of free space

What is a capacitor?

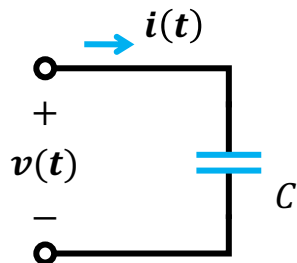


The charge on the capacitor $q = \mathbf{C}v(t)$

CAPACITANCE is defined as
ratio of charge, $q(t)$, “stored” on conductors to
potential difference, $v(t)$, between them

Current CANNOT actually flow through a capacitor

What is a capacitor?

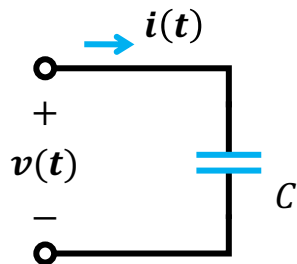

$$q = Cv(t)$$

The charge on the capacitor $q(t) = Cv(t)$


According to the define of current $i(t) = \frac{dq(t)}{dt}$

The current-voltage terminal characteristics of capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

A capacitor is an open circuit at DC

What is a capacitor?

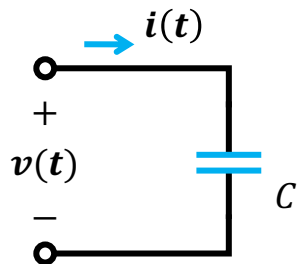

$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$dv(t) = \frac{1}{C} i dt$$


$$v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx = \frac{1}{C} \int_{-\infty}^{t_0} i(x) dx + \frac{1}{C} \int_{t_0}^t i(x) dx$$

$$= v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$



The voltage due to the charge accumulated on C from time $t = -\infty$ to time $t = t_0$

What is a capacitor?

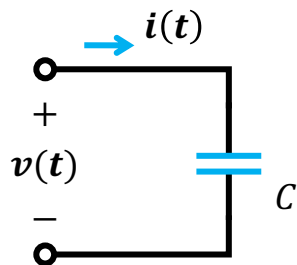

$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

$$v(t + \Delta t) - v(t) = \frac{1}{C} \int_t^{t+\Delta t} i(\tau) d\tau$$

$$|v(t + \Delta t) - v(t)| \geq 0$$


$$\left| \frac{1}{C} \int_t^{t+\Delta t} i(\tau) d\tau \right| \leq \frac{1}{C} \int_t^{t+\Delta t} |i(\tau)| d\tau$$

$$\leq \frac{1}{C} \int_t^{t+\Delta t} I_{max} d\tau = \frac{1}{C} I_{max} \Delta t \xrightarrow{\Delta t \rightarrow 0} 0$$

$$0 \leq |v(t + \Delta t) - v(t)| \leq 0$$

Voltage on capacitor CANNOT change abruptly

What is a capacitor?

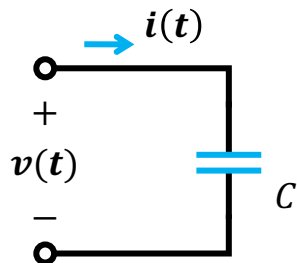

POWER delivered to a capacitor

$$p(t) = v(t)i(t) = Cv(t) \frac{dv(t)}{dt}$$

ENERGY stored in the electric field

$$q = Cv(t)$$


$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

$$w(t) = \int_{-\infty}^t Cv(\tau) \frac{dv(\tau)}{d\tau} d\tau = \frac{1}{2} Cv^2(\tau) \Big|_{v(-\infty)}^{v(t)} = \frac{1}{2} Cv^2(t)$$

Example 1

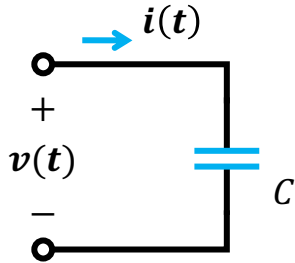QUESTION: Find the voltage on the capacitor, $v(t)$, with $i(t)$ changes as a step function





$$i(t) = \begin{cases} 0 & t \leq 0 \\ I_0 & t > 0 \end{cases}$$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(x) dx$$


If $v(0) = 0$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ \frac{I_0 t}{C} & t > 0 \end{cases}$$

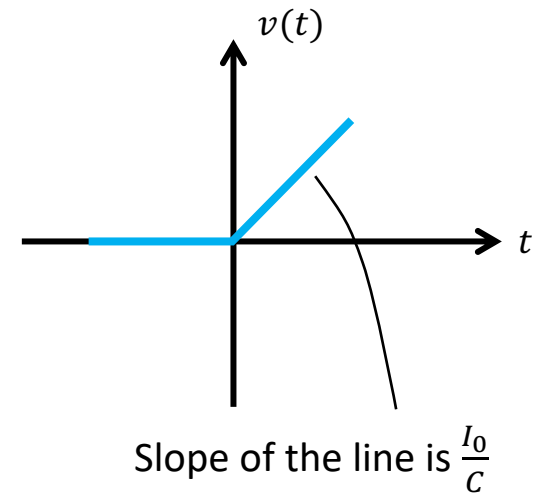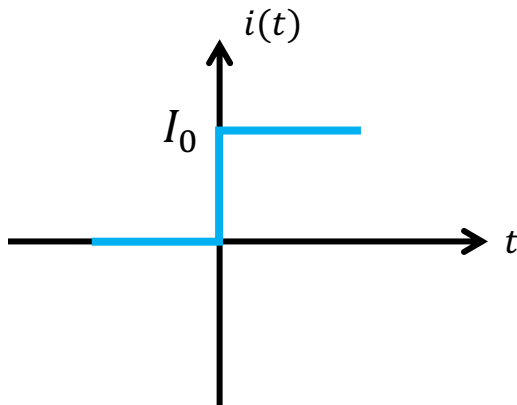



Example 2

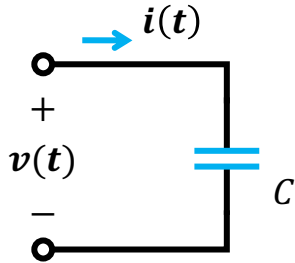QUESTION: Find the current across the capacitor, $i(t)$, with $v(t)$ changes as a step function



$$v(t) = \begin{cases} 0 & t \leq 0 \\ V_0 & t > 0 \end{cases}$$

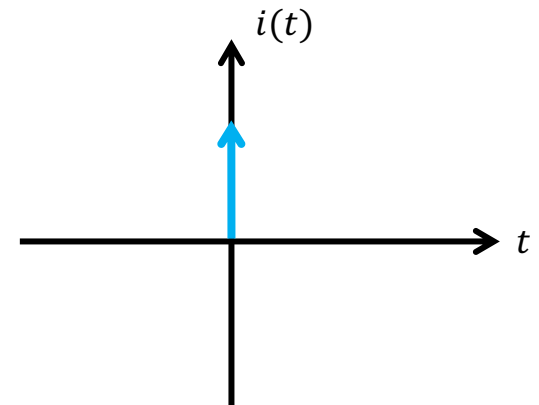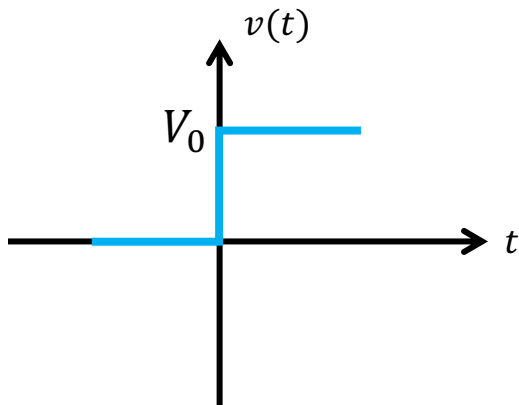
$$i(t) = \frac{dv(t)}{dt} = V_0 \delta(t)$$



Outlines

■ Capacitor

- What is a capacitor


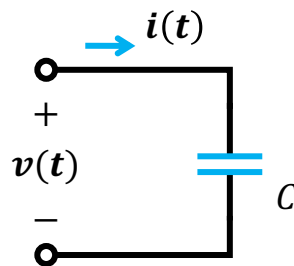


$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

Capacitors in series

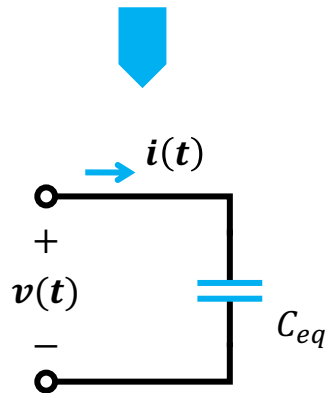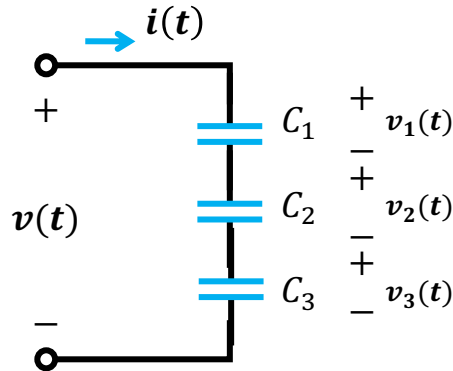

According to i - v characteristic of a capacitor

$$i(t) = C_1 \frac{dv_1(t)}{dt} = C_2 \frac{dv_2(t)}{dt} = C_3 \frac{dv_3(t)}{dt}$$

$$i(t) = C_{eq} \frac{dv(t)}{dt}$$

According to KVL


$$i(t) = C_{eq} \frac{d}{dt} (v_1(t) + v_2(t) + v_3(t))$$

$$= C_{eq} i(t) \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Review: resistors in series

VOLTAGE DIVIDER

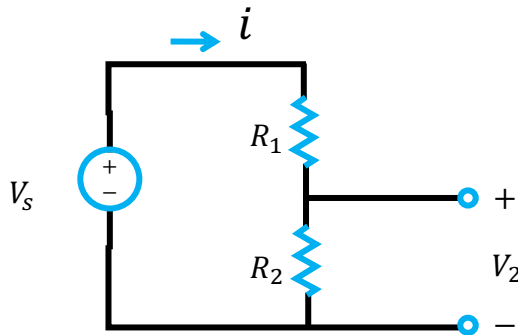

According to KVL $V_s = iR_1 + iR_2$

$$\rightarrow i = \frac{V_s}{R_1 + R_2}$$

$$V_2 = iR_2 = \frac{R_2}{R_1 + R_2} V_s$$


Voltage divided
over resistors

- **Equivalent resistance, R_{eq} , (series) is sum of resistances**
- **Voltage difference across a single resistance of resistors in series**

$$R_{eq} = \sum_{i=1}^N R_i$$

$$V_i = \frac{R_i}{R_{eq}} V_s$$

Voltage divider for capacitors

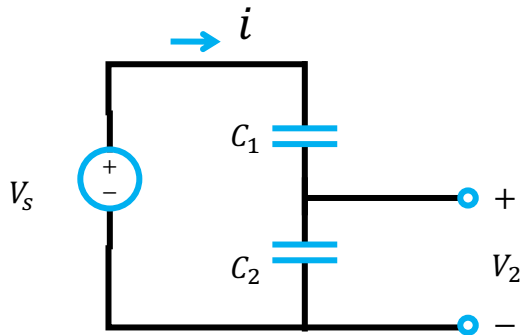


According to KVL


$$\begin{aligned} V_s &= v_1(t) + v_2(t) \\ &= \frac{1}{C_1} \int i(t) dt + \frac{1}{C_2} \int i(t) dt \end{aligned}$$

$$\Rightarrow \begin{cases} v_1(t) = \frac{C_2}{C_1 + C_2} v(t) \\ v_2(t) = \frac{C_1}{C_1 + C_2} v(t) \end{cases}$$

Voltage divider


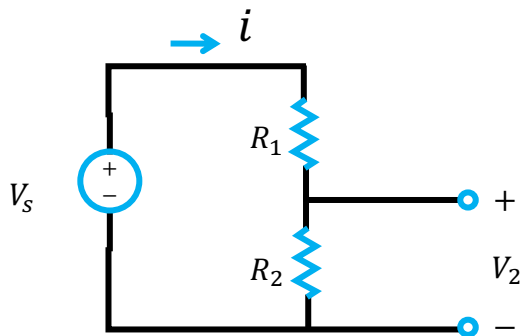

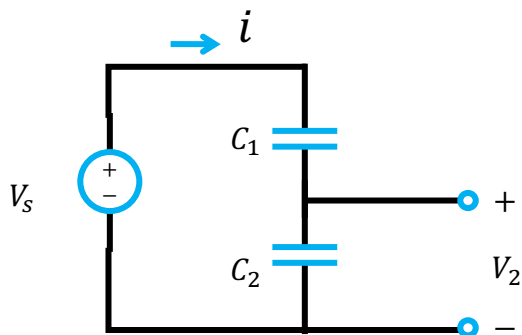
$$\begin{cases} v_1(t) = \frac{R_1}{R_1 + R_2} v(t) \\ v_2(t) = \frac{R_2}{R_1 + R_2} v(t) \end{cases}$$



$$\begin{cases} v_1(t) = \frac{C_2}{C_1 + C_2} v(t) \\ v_2(t) = \frac{C_1}{C_1 + C_2} v(t) \end{cases}$$

Capacitors in parallel

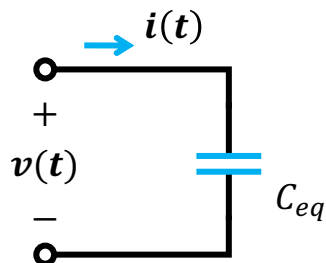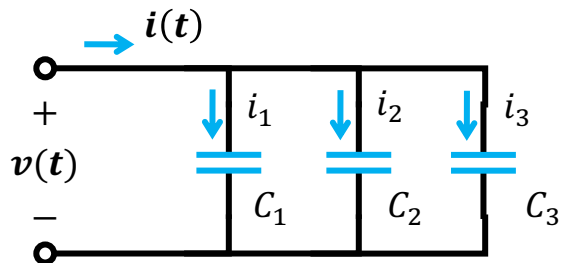

According to KCL

$$i(t) = i_1(t) + i_2(t) + i_3(t)$$

According i - v characteristic of a capacitor

$$\begin{aligned} i(t) &= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + C_3 \frac{dv(t)}{dt} \\ &= (C_1 + C_2 + C_3) \frac{dv(t)}{dt} \end{aligned}$$

For the equivalent circuit


$$i(t) = C_{eq} \frac{dv(t)}{dt}$$



$$C_{eq} = C_1 + C_2 + C_3$$

Example 3

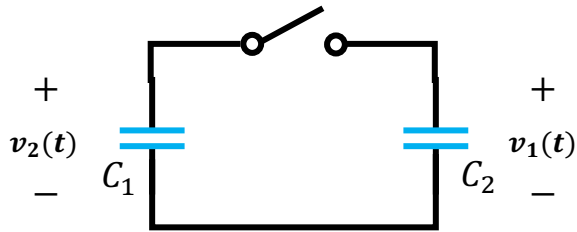QUESTION: Find the total energy stored in the two capacitors before & after the switch is closed, if the charges on the two capacitors at $t = 0$ are $q_1(0) = Q_1$ and $q_2(0) = Q_2$, respectively.




- BEFORE the switch is turned on ($t < 0$)
total energy stored in the two capacitors

$$w(t < 0) = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2}$$

Example 3

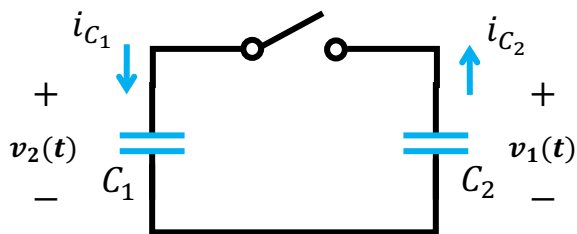QUESTION: Find the total energy stored in the two capacitors before & after the switch is turned on, if the charges on the two capacitors at $t = 0$ are $q_1(0) = Q_1$ and $q_2(0) = Q_2$, respectively.



$$w(t < 0) = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2}$$

- AFTER the switch is turned on ($t \geq 0$)

Assume the circuit is in steady state @ $t = t_1$

According to KVL


$$v_1(t) = v_2(t) \quad \Rightarrow \quad \frac{q_1(t)}{C_1} = \frac{q_2(t)}{C_2}$$

According to conservation of charge

$$q_1(t) + q_2(t) = Q_1 + Q_2$$

Example 3

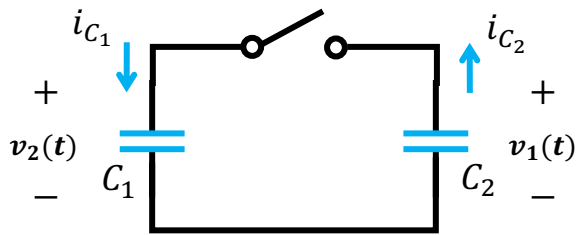
QUESTION: Find the total energy stored in the two capacitors before & after the switch is turned on, if the charges on the two capacitors at $t = 0$ are $q_1(0) = Q_1$ and $q_2(0) = Q_2$, respectively.



$$w(t < 0) = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2}$$


- AFTER the switch is turned on ($t \geq 0$). Assume the circuit is in steady state @ $t = t_1$

$$\begin{cases} \frac{q_1(t)}{C_1} = \frac{q_2(t)}{C_2} \\ q_1(t) + q_2(t) = Q_1 + Q_2 \end{cases}$$


$$\begin{cases} q_1(t_1) = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2) \\ q_2(t_1) = \frac{C_2}{C_1 + C_2} (Q_1 + Q_2) \end{cases}$$

Example 3

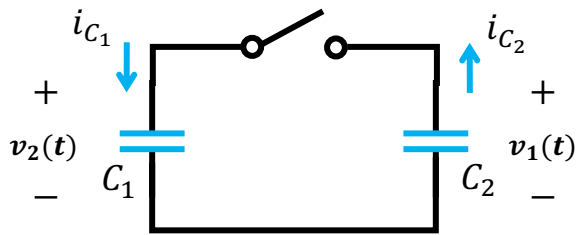QUESTION: Find the total energy stored in the two capacitors before & after the switch is turned on, if the charges on the two capacitors at $t = 0$ are $q_1(0) = Q_1$ and $q_2(0) = Q_2$, respectively.




$$w(t < 0) = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2}$$

- AFTER the switch is turned on ($t \geq 0$). Assume the circuit is in steady state @ $t = t_1$

$$\begin{aligned} w(t_1) &= \frac{q_1^2(t)}{2C_1} + \frac{q_2^2(t)}{2C_2} \\ &= \frac{1}{2C_1} \left(\frac{C_1}{C_1 + C_2} (Q_1 + Q_2) \right)^2 + \\ &\quad \frac{1}{2C_2} \left(\frac{C_2}{C_1 + C_2} (Q_1 + Q_2) \right)^2 \\ &= \frac{(Q_1 + Q_2)^2}{2(C_1 + C_2)} \end{aligned}$$

Example 3

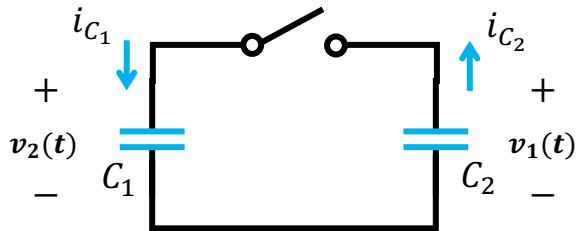QUESTION: Find the total energy stored in the two capacitors before & after the switch is turned on, if the charges on the two capacitors at $t = 0$ are $q_1(0) = Q_1$ and $q_2(0) = Q_2$, respectively.



- BEFORE the switch is turned on ($t < 0$)

$$w(t < 0) = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2}$$

- AFTER the switch is turned on ($t \geq 0$). Assume the circuit is in steady state @ $t = t_1$


$$w(t_1) = \frac{(Q_1 + Q_2)^2}{2(C_1 + C_2)}$$

WHY $w(t < 0) \neq w(t_1)$?

Outlines

■ Capacitor

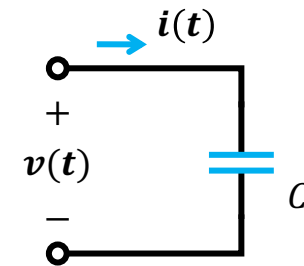- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider



$$q = Cv(t)$$


$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$


■ Inductor

What is an inductor

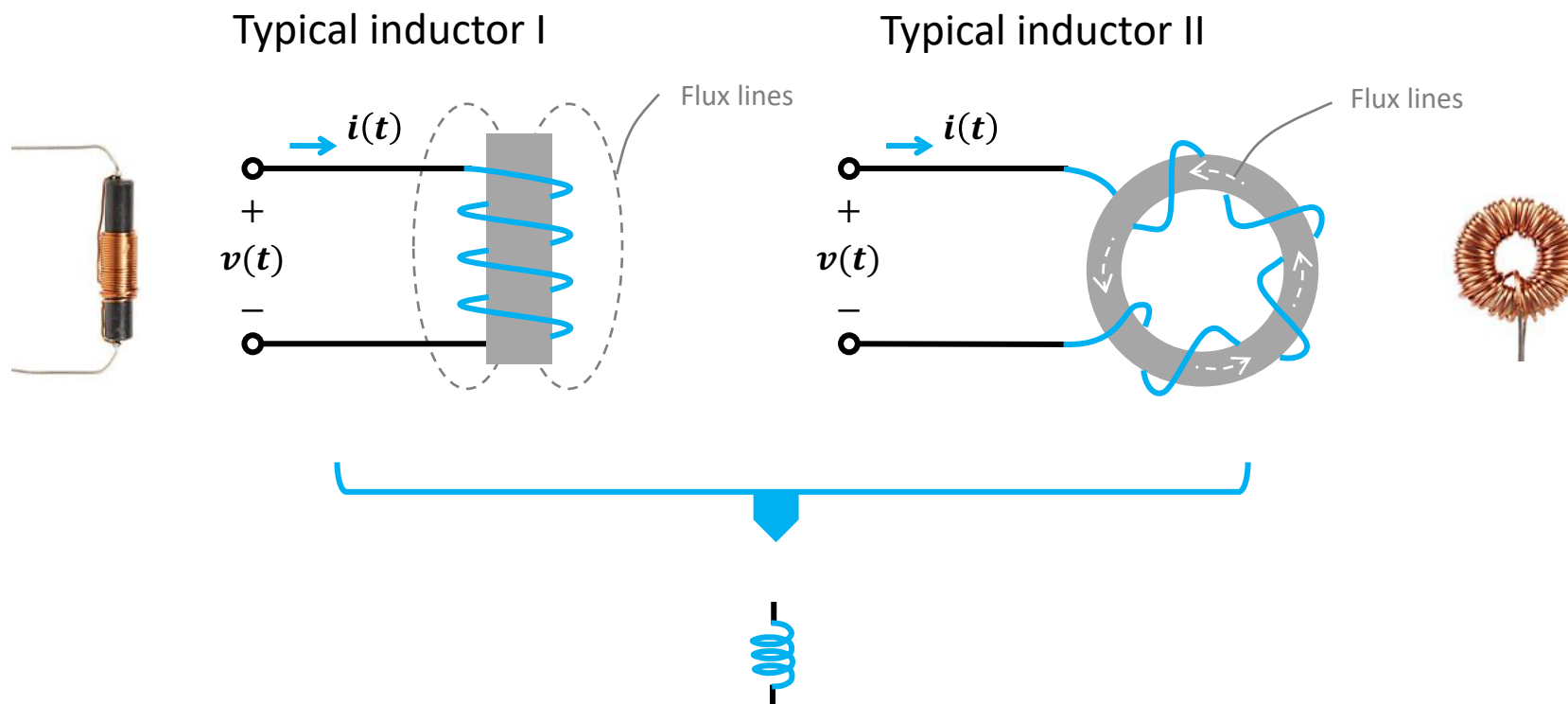An INDUCTOR is a circuit element that consists of a conducting wire usually in the form of a coil.



Recall: high school physics

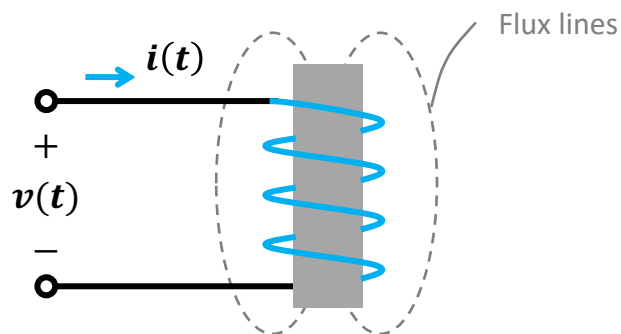

AMPÈRE'S LAW

The **magnetic field**, B , created by an **electric current**, I , is proportional to the size of that electric current with a constant of proportionality equal to the permeability of free space, μ_0 .


$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \left(I + \varepsilon_0 \frac{d\Phi_E}{dt} \right)$$

FARADAY'S LAW

The **electromotive force**, ε , or EMF is proportional to the rate of change of **magnetic flux**, Φ , through a loop to the magnitude of the electro-motive force induced in the loop.

$$\varepsilon = \frac{d\Phi}{dt}$$


What is an inductor

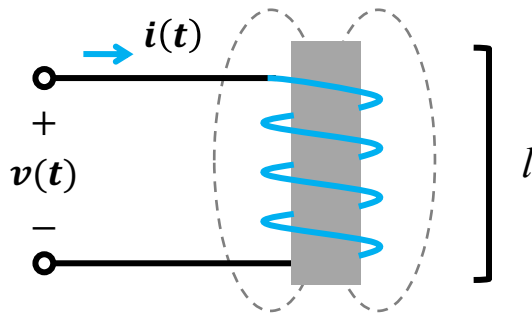

- Step 1: current $i(t)$ pass through the wire
- Step 2: magnetic flux ϕ is generated in the wire
- Step 3: if the wire is coiled, the flux linkage for the coil is

$$\lambda(t) = N\phi$$

What is an inductor

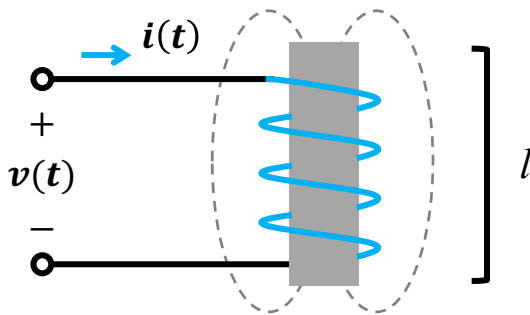

For linear system

$$\lambda(t) = Li(t)$$

According to Faraday's Law


$$v(t) = \frac{d\lambda(t)}{dt} = \frac{dLi(t)}{dt}$$

The current-voltage terminal characteristics of inductor

$$v(t) = L \frac{di(t)}{dt}$$

An inductor is a short circuit at DC

What is an inductor

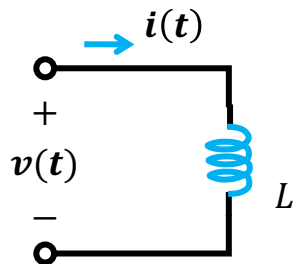

INDUCTANCE is defined as


ratio of voltage, $v(t)$, across the coils to time rate of change of current flowing, $i(t)$, through it

$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

- The unit of inductance: **henry (H)**
- More frequently used: **nH**

What is an inductor

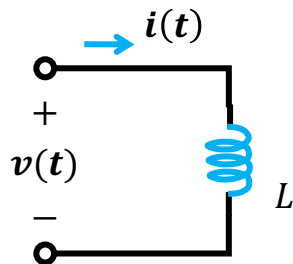

$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$di(t) = \frac{1}{L} v(t) dt$$


$$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx = \frac{1}{L} \int_{-\infty}^{t_0} v(x) dx + \frac{1}{L} \int_{t_0}^t v(x) dx$$

$$= \frac{1}{L} \lambda(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$



The flux linkage due to the charge accumulated on L from time $t = -\infty$ to time $t = t_0$

What is an inductor

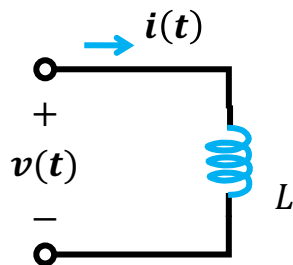

$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

$$i(t + \Delta t) - i(t) = \frac{1}{L} \int_t^{t+\Delta t} v(\tau) d\tau$$

$$|i(t + \Delta t) - i(t)| \geq 0$$


$$\left| \frac{1}{L} \int_t^{t+\Delta t} v(\tau) d\tau \right| \leq \frac{1}{L} \int_t^{t+\Delta t} |v(\tau)| d\tau$$

$$\leq \frac{1}{L} \int_t^{t+\Delta t} V_{max} d\tau = \frac{1}{L} V_{max} \Delta t \xrightarrow{\Delta t \rightarrow 0} 0$$

$$0 \leq |i(t + \Delta t) - i(t)| \leq 0$$

Current through inductor CANNOT change instantaneously

What is an inductor

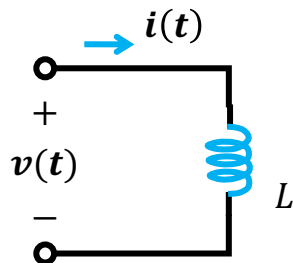

POWER delivered to an inductor

$$p(t) = v(t)i(t) = Li(t) \frac{di(t)}{dt}$$

ENERGY stored in the electric field

$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$


$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

$$w(t) = \int_{-\infty}^t Li(\tau) \frac{di(\tau)}{dt} d\tau = \frac{1}{2} Li^2(\tau) \Big|_{i(-\infty)}^{i(t)} = \frac{1}{2} Li^2(t)$$

Outlines

■ Capacitor

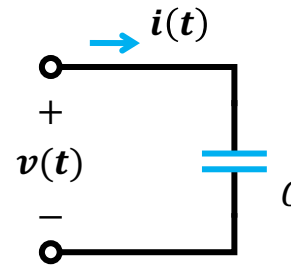- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

- What is an inductor


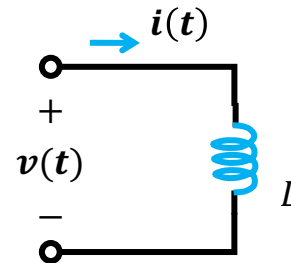


$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

Inductor in series

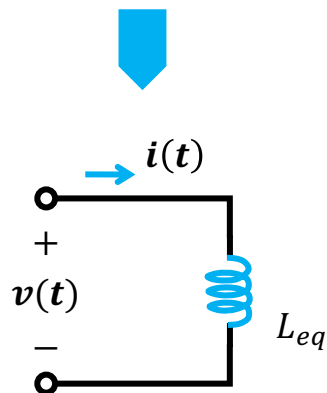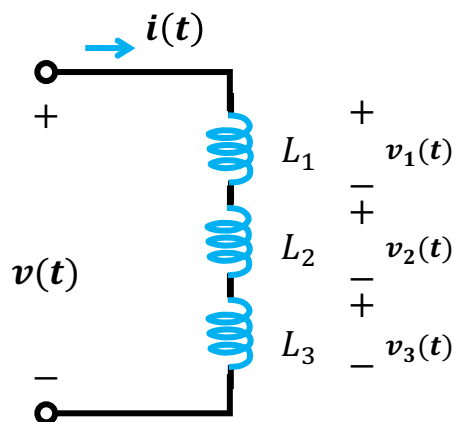

According to KVL

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

According i - v characteristic of an inductor

$$\begin{aligned} v(t) &= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + L_3 \frac{di(t)}{dt} \\ &= (L_1 + L_2 + L_3) \frac{di(t)}{dt} \end{aligned}$$

For the equivalent circuit


$$v(t) = L_{eq} \frac{di(t)}{dt}$$



$$L_{eq} = L_1 + L_2 + L_3$$


Inductors in parallel

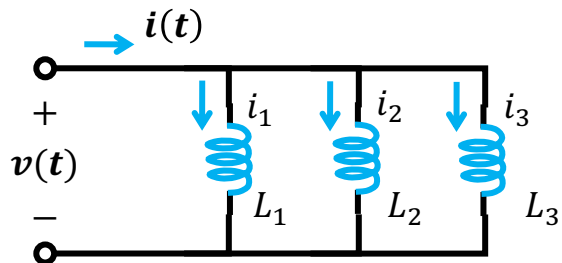According i - v characteristic of an inductor




$$v(t) = L_1 \frac{di_1(t)}{dt} = L_2 \frac{di_2(t)}{dt} = L_3 \frac{di_3(t)}{dt}$$
$$v(t) = L_{eq} \frac{di(t)}{dt}$$

According to KVL

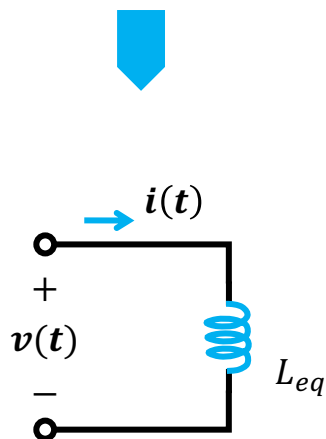

$$v(t) = L_{eq} \frac{d}{dt} (i_1(t) + i_2(t) + i_3(t))$$


$$= L_{eq} i(t) \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)$$


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Outlines

■ Capacitor

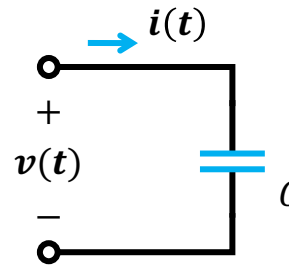- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

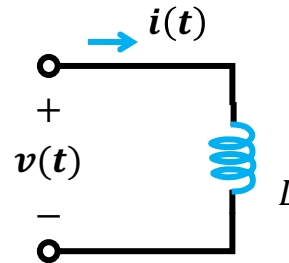- What is an inductor
- Inductors in series/parallel






$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$


Resistor v.s. Capacitor v.s. Inductor

			
i - v characteristic	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
v - i characteristic	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
p (power transferred in)	$p = vi$	$p = vi$	$p = vi$
w (stored energy)	0	$w = \frac{1}{2} C v^2(t)$	$w = \frac{1}{2} L i^2(t)$
Series combination	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel combination	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
DC behavior	NO	open circuit	short circuit
Instantaneous change of v	\checkmark	\times	\checkmark
Instantaneous change of i	\checkmark	\checkmark	\times

Outlines

■ Capacitor

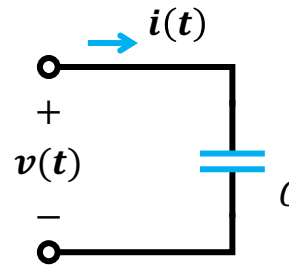- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

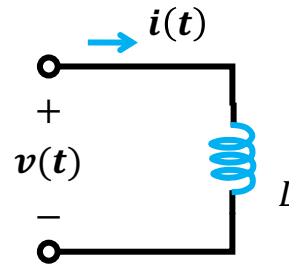- What is an inductor
- Inductors in series/parallel
- Resistor v.s. capacitor v.s. inductor




$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

■ Magnetically coupled networks

What if there is one coil


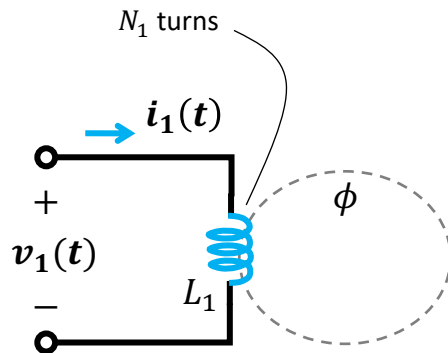


According to AMPÈRE'S LAW, consider the ideal situation

- Flow of electric current will create a magnetic field
- The flux linkage for the coil is $\lambda_1(t) = N_1\phi = L_1i_1$

For the ideal inductor $v_1(t) = L_1 \frac{di_1(t)}{dt}$

What if two coils closed to each other

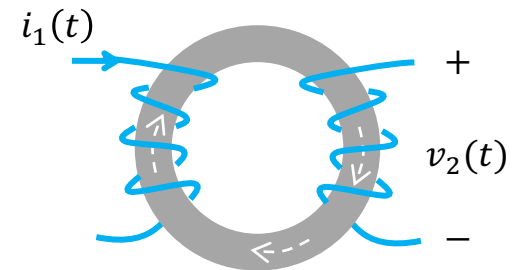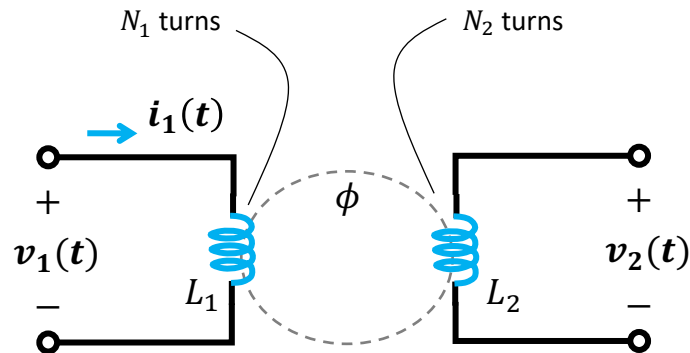



According to FARADAY'S LAW,

- The flux linkage for the coil N_2 is $\lambda_2(t) = N_2\phi = N_2 \frac{\lambda_1}{N_1} = N_2 \frac{L_1 i_1}{N_1}$
- Voltage will be induced

$$v_2(t) = \frac{d\lambda_2(t)}{dt} = \frac{d}{dt} \left(N_2 \frac{L_1 i_1}{N_1} \right) = \boxed{\frac{N_2}{N_1} L_1} \frac{di_1}{dt}$$

L_{21} , mutual inductance

Mutual inductance

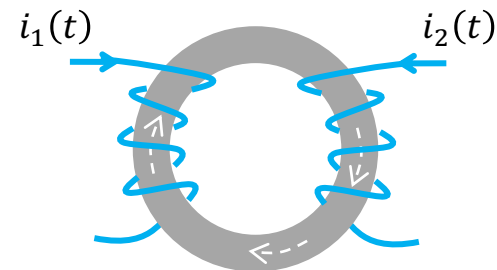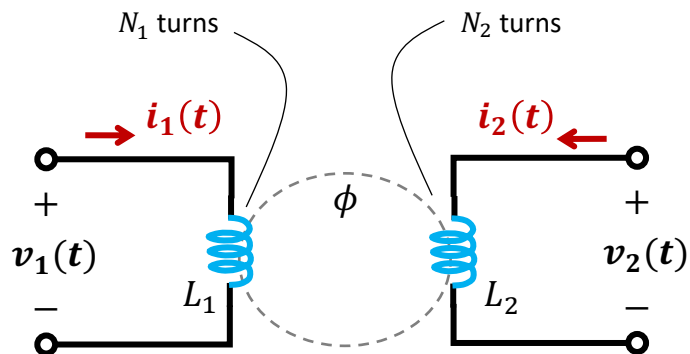


- The flux linkages for each coil

$$\begin{cases} \lambda_1 = L_1 i_1 + L_{12} i_2 \\ \lambda_2 = L_{21} i_1 + L_2 i_2 \end{cases}$$

- The current-voltage relationship

$$\begin{cases} v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt} \\ v_2 = \frac{d\lambda_2}{dt} = L_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

Mutual inductance

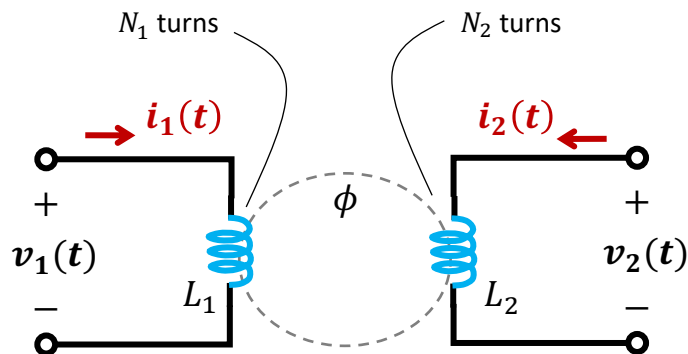

$$\begin{cases} v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt} \\ v_2 = \frac{d\lambda_2}{dt} = L_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

- Self-inductances L_1, L_2 , and mutual inductance L_{12}, L_{21}
- For LINEAR SYSTEM $L_{12} = L_{21} = M$


$$\Rightarrow \begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

a self term due to $i_1(t)$

a mutual term due to $i_2(t)$


Mutual inductance

- Case 1: both currents enter the dots

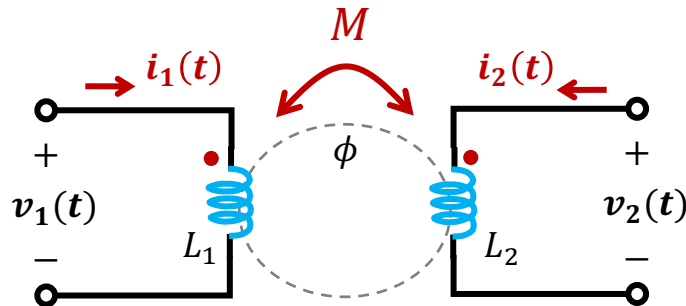

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

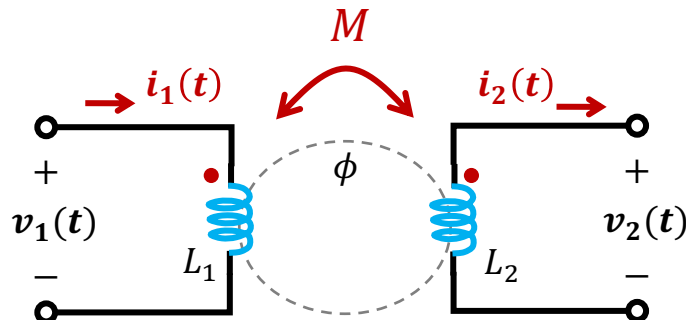
- Case 2: one current enters the dot, the other leaves the dot



$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

Example 4

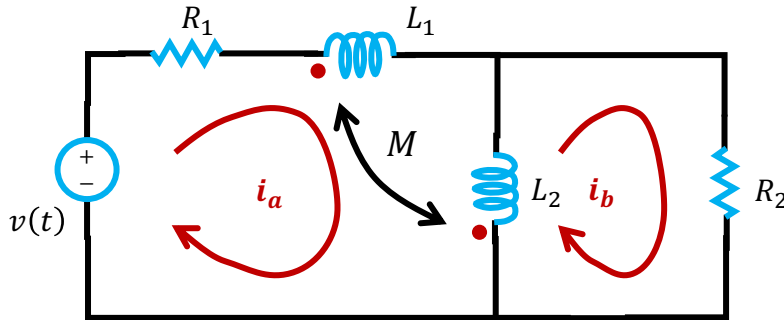QUESTION: write the equations for the circuit




- According to KVL

$$\left\{ \begin{array}{l} v(t) = \underbrace{R_1 i_a}_{\text{self term of } L_1} + \underbrace{L_1 \frac{di_a}{dt}}_{\text{self term of } L_1} + \underbrace{M \frac{d}{dt}(i_b - i_a)}_{\text{mutual term due to } L_2} + \underbrace{L_2 \frac{d}{dt}(i_a - i_b)}_{\text{self term of } L_2} - \underbrace{M \frac{di_a}{dt}}_{\text{mutual term due to } L_1} \\ L_2 \frac{d}{dt}(i_b - i_a) + M \frac{di_a}{dt} + R_2 i_b = 0 \end{array} \right.$$

Outlines

■ Capacitor

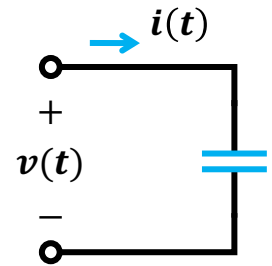- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

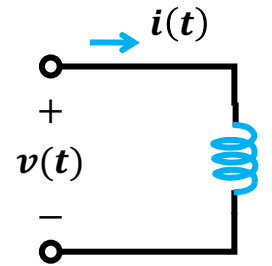- What is an inductor
- Inductors in series/parallel
- Resistor v.s. capacitor v.s. inductor




$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$


$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

■ Magnetically coupled networks

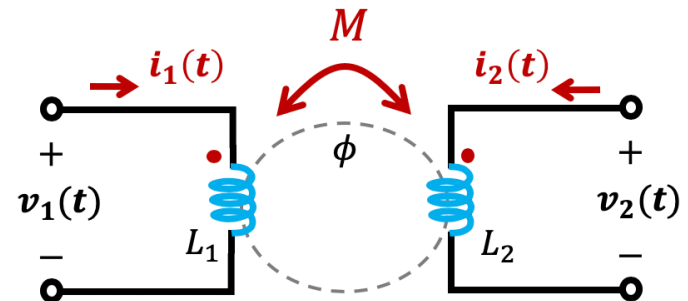- What is mutual inductance
- **Power & Energy**



Power & Energy

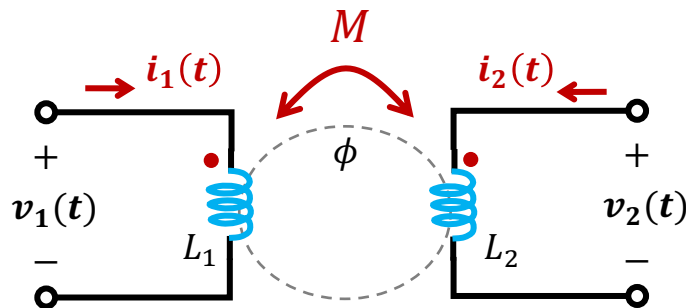

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$


- The total power generated by the network

$$p(t) = v_1(t)i_1(t) + v_2(t)i_2(t)$$

$$= \left(L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) i_1(t) + \left(M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \right) i_2(t)$$

$$= \frac{1}{2} L_1 \frac{d}{dt} i_1^2(t) + \frac{1}{2} L_2 \frac{d}{dt} i_2^2(t) + M \frac{d}{dt} (i_1(t)i_2(t))$$

Power & Energy

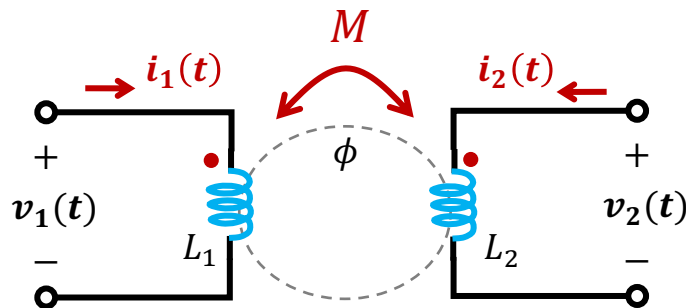

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$


- The total power generated by the network

$$p(t) = \frac{1}{2} L_1 \frac{d}{dt} i_1^2(t) + \frac{1}{2} L_2 \frac{d}{dt} i_2^2(t) + M \frac{d}{dt} (i_1(t) i_2(t))$$

- The total energy stored in the network

$$w(t) = \int_{-\infty}^t p(\tau) d\tau = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$$

Power & Energy

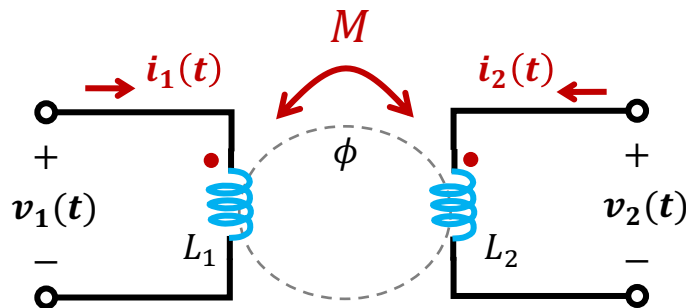

$$\begin{cases} v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{cases}$$

$$\begin{aligned} w(t) &= \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t) \\ &= \frac{1}{2} \left(L_1 - \frac{M^2}{L_2} \right) i_1^2 + \frac{1}{2} L_2 \left(i_2 + \frac{M}{L_2} i_1 \right)^2 \end{aligned}$$

Since $w(t) \geq 0$ must be guaranteed


$$\Rightarrow M \leq \sqrt{L_1 L_2}$$

DEFINE the coefficient of coupling between 2 inductors $k = \frac{M}{\sqrt{L_1 L_2}}$

Outlines

■ Capacitor

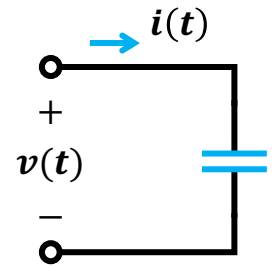- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

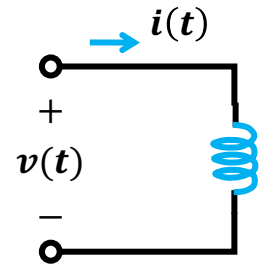- What is an inductor
- Inductors in series/parallel
- Resistor v.s. capacitor v.s. inductor




$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$


$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

■ Magnetically coupled networks

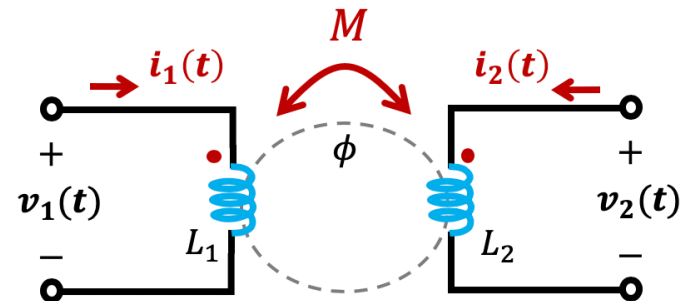
- What is mutual inductance
- Power & Energy
- **Ideal transformer**



Ideal Transformer

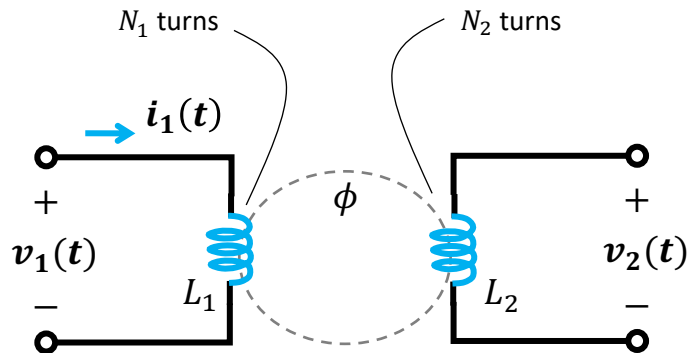

Symbol of IDEAL TRANSFORMER

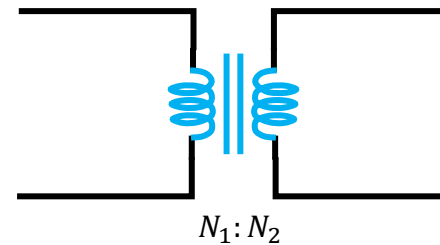


Ideal case

- The core flux, ϕ , links **ALL** the turns of both coils
- There is **NO** wire resistance

$$\begin{cases} v_1 = N_1 \frac{d\phi}{dt} \\ v_2 = N_2 \frac{d\phi}{dt} \end{cases} \quad \Rightarrow \quad \frac{v_1}{v_2} = \frac{N_1}{N_2} \text{ is DEFINED as turns ratio}$$

Ideal Transformer

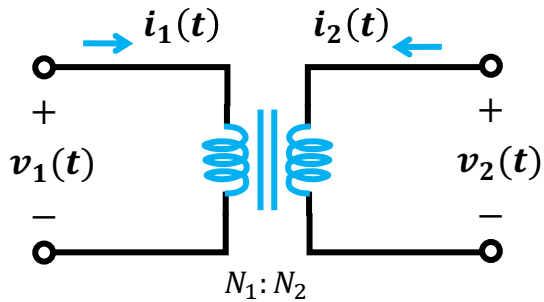

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$


- $i_2(t)$ is generated from coupling
- According to Ampère's LAW

$$N_1 i_1 + N_2 i_2 = 0$$

Outlines

■ Capacitor

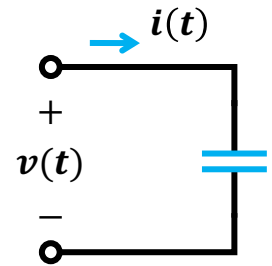- What is a capacitor
- Capacitors in series/parallel
- Capacitors voltage divider




$$q = Cv(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

■ Inductor

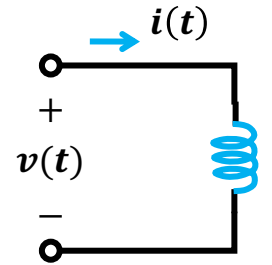- What is an inductor
- Inductors in series/parallel
- Resistor v.s. capacitor v.s. inductor




$$\lambda(t) = Li(t)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

■ Magnetically coupled networks

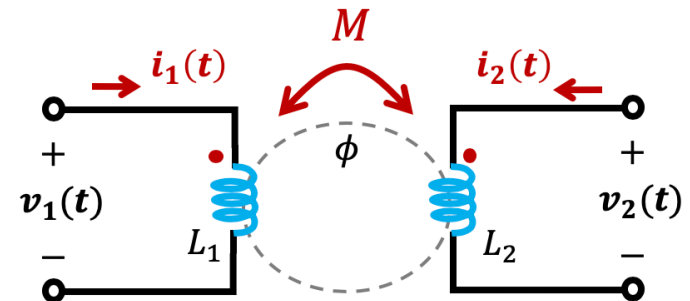- What is mutual inductance
- Power & Energy
- Ideal transformer



Reading tasks & learning goals

- Reading tasks

- Basic Engineering Circuit Analysis, 10th edition
 - Chapter 6 and 10

- Learning goals

- Be able to calculate **V/I** for capacitor/inductor
- Be able to calculate **stored energy** for capacitor/inductor
- Be able to combine cap./ind. in series/parallel
- Understand the concepts of mutual inductance, coefficient of coupling, and turns ratio